

Jeremy Scheuerman

Dr. Franchi

COSC 250

1 May 2021

Assignment 13 (Last Part)

Designing A memory Cell:

Well Obviously this would involve a system of Fetch and Store to transmit and read the data, and the data would also be wiped on turning the system off.

It would involve Nor gates and a flip flop circuit more specifically the R-S flip flop (Reset flip flop)

Diagram of 4x4

